
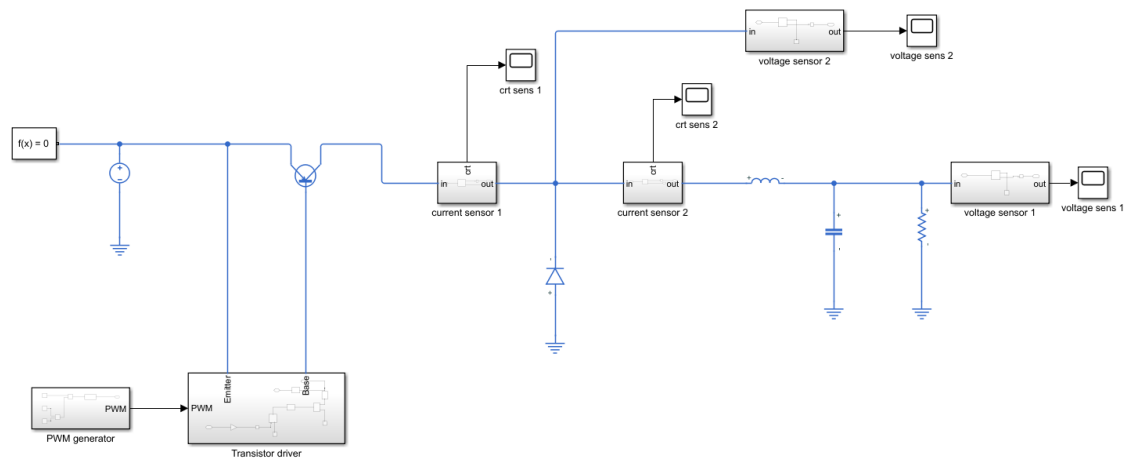


# PROJECT PART IV

## A. Ideal simulation

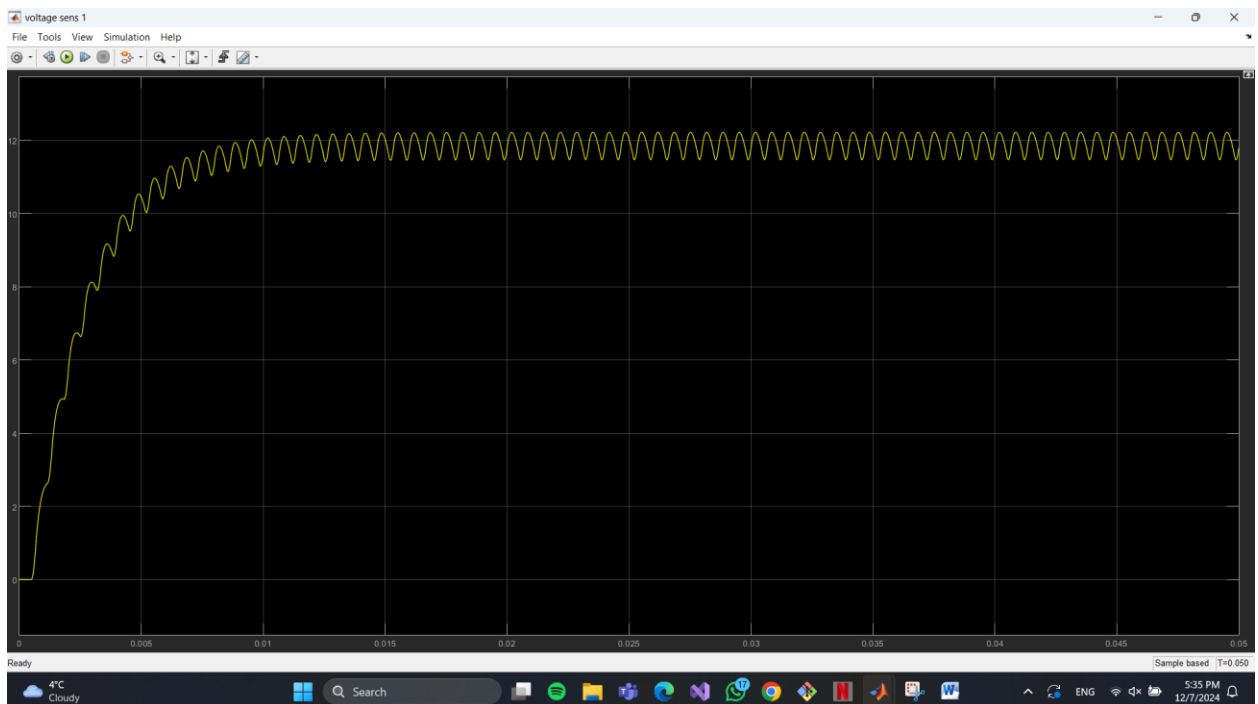

Output voltage graph:



Diode

☒ Auto Apply

Settings	Description
----------	-------------

NAME

VALUE

Parameters

> Forward voltage	0.1	V
> On resistance	0.001	Ohm
> Off conductance	1e-8	1/Ohm

Initial Targets

Nominal Values

Inductor

☒ Auto Apply

Settings	Description
----------	-------------

NAME

VALUE

Parameters

> Inductance	L	0.006	H	⌵
> Series resistance	0		Ohm	⌵
> Parallel conductance	1e-9		1/Ohm	⌵

Initial Targets

Nominal Values

Capacitor ☒ Auto Apply

Settings Description

NAME VALUE

✓ Parameters

> Capacitance	C	0.000104	F
> Series resistance	1e-6		Ohm
> Parallel conductance	0		1/Ohm

> Initial Targets

> Nominal Values

Resistor ☒ Auto Apply

Settings Description

NAME VALUE

✓ Parameters

> Resistance	R	2.4	Ohm
--------------	---	-----	-----

> Initial Targets


> Nominal Values

Code:


```
U_in = 48;  
U_out = 12;  
frequency = 1500;  
R = 2.4;
```

```
L = 0.006;  
C = 0.000104;  
I_out = 5;
```

## B. With residual elements

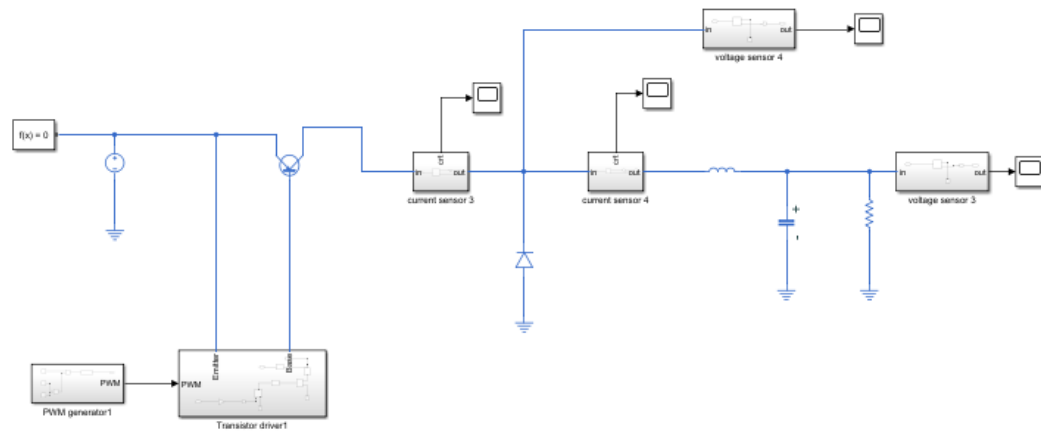

Output voltage graph:

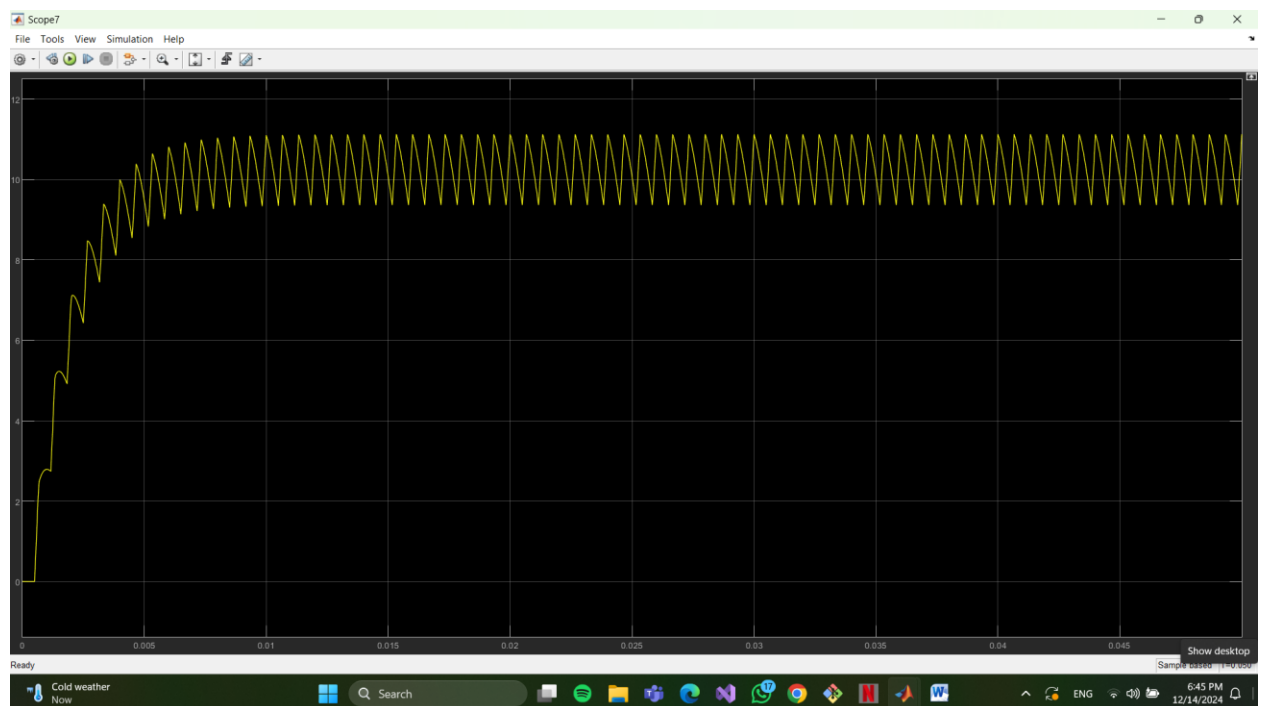

Diode

☒ Auto Apply

SettingsDescription

NAMEVALUE

Parameters

> Forward voltage670mV

> On resistance0.3Ohm

> Off conductance1e-81/Ohm

> Initial Targets

> Nominal Values

Capacitor

☒ Auto Apply

SettingsDescription

NAMEVALUE

Main

Capacitance modelConstant

> Capacitance100uF

Tolerance applicationApply minimum tolerance value

> Capacitance tolerance (%)20

> Series resistance2.86624Ohm

> Parallel conductance01/Ohm

> Operating Limits

> Initial Targets

> Nominal Values

> Faults

Inductor

☒ Auto Apply ?

Settings	Description	
NAME	VALUE	
▼ Main		
> Inductance	6	mH ▼
Tolerance application	Apply minimum tolerance value ▼	
> Tolerance (%)	20	
> Series resistance	46	mOhm ▼
> Parallel conductance	1e-9	1/Ohm ▼
> Operating Limits		
> Initial Targets		
> Nominal Values		
> Faults		

Observations based on comparison of performances:

- Output voltage:

In the ideal simulation, there are no losses or tolerances so the output voltage closely matches the target value.

The output voltage in the system with residual elements deviates a little because of losses like diode forward voltage, ESR in the capacitor, and DCR in the inductor.

- Efficiency:

Since there are no power losses, the ideal system operates as efficiently as possible.

In the residual system the efficiency is reduced because of: power losses related to tolerances, energy dissipation across the diode, inductor and capacitor resistances.

- Effect of tolerances:

The stability of the system is directly impacted by tolerances in the inductor and capacitor.

Inductor tolerance: results in subtle variations of energy which slightly affects the output voltage stability.

Capacitor tolerance: causes an increased ripple.

- Conclusions:

The ideal simulation provides a foundation for the system's optimal performance.

The residual simulation highlights the real limitations of the system, underlining the impact of component properties and tolerances on performance.